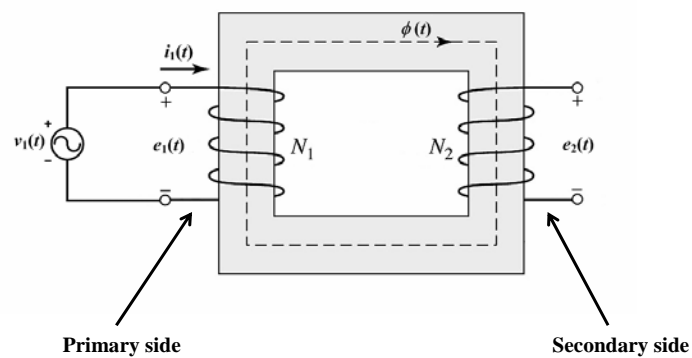


II. Transformers


Transformer

Transformer comprises two or more windings coupled by a common magnetic circuit (M.C.).

If the primary side is connected to an AC voltage source $v_1(t)$, an AC flux $\phi(t)$ will be produced in the M.C.



Ideal transformer voltage relationship

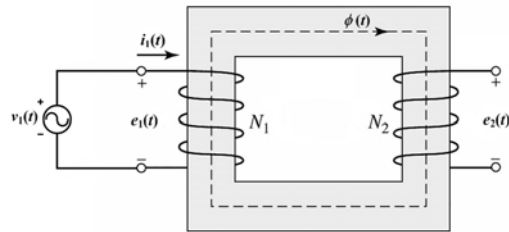


$$e_1(t) = N_1 \frac{d\phi(t)}{dt}$$


$$e_2(t) = N_2 \frac{d\phi(t)}{dt}$$

$$\frac{e_1}{e_2} = \frac{N_1}{N_2}$$


Ideal transformer symbol

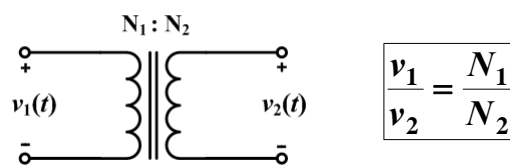


Another representation

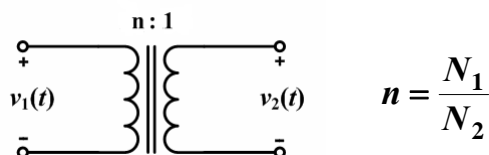


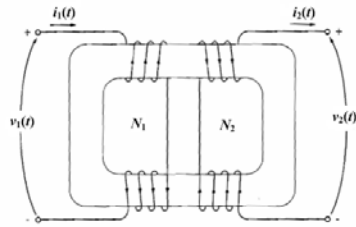
There are two common types of transformer construction:



(a) core-type


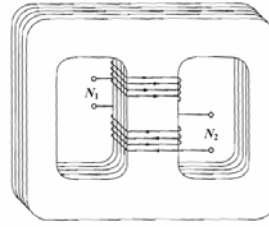


(b) shell-type

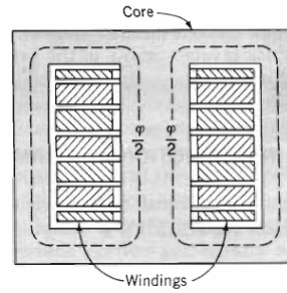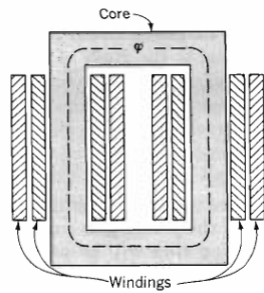


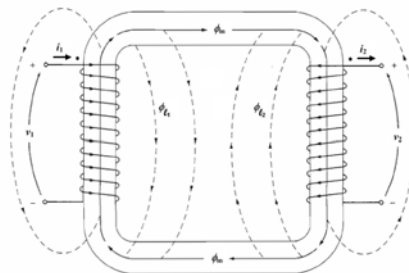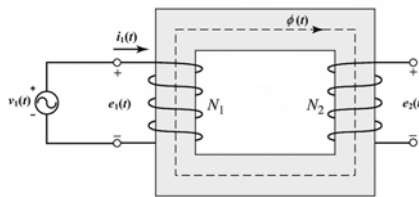1. Analysis of the transformer with no-load

Secondary side open-circuited:
(no sec. current)




Modelling of Magnetic Core

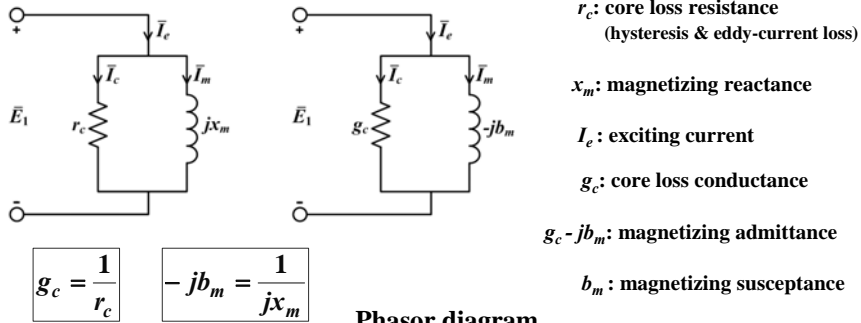

$$g_c = \frac{1}{r_c} \quad -jb_m = \frac{1}{jx_m}$$

Phasor diagram

$$\vec{I}_e = \vec{I}_c + \vec{I}_m$$

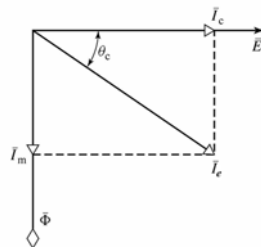


\vec{I}_m lags \vec{E}_1 by 90°
 \vec{I}_c in phase with \vec{E}_1

Modelling of Leakage Flux

Let us express the voltage drop due to leakage flux in the primary winding below

$$v_{\ell_1} = \frac{d\lambda_{\ell_1}}{dt} = \frac{d\lambda_{\ell_1}}{di_e} \frac{di_e}{dt} = L_{\ell_1} \frac{di_e}{dt} \quad \text{where} \quad \lambda_{\ell_1} = N_1 \phi_{\ell_1}$$

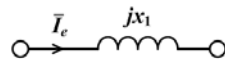
$$v_{\ell_1} = L_{\ell_1} \frac{di_e}{dt} \quad L_{\ell_1} : \text{leakage inductance of primary winding}$$



primary leakage reactance: $x_1 = \omega L_{\ell_1}$


$$\omega = 2\pi f$$

Modelling of Copper Loss

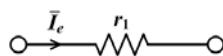

r_1 : resistance of primary winding

Equivalent circuit model of primary side

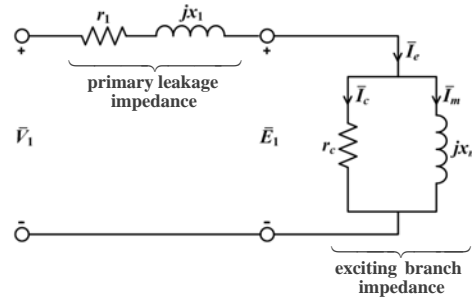

Exciting current is only a few percent of rated primary current of the transformer

2. Ideal Transformer Operation

- No leakage fluxes
- Negligible winding internal resistances
- B-H characteristic of the magnetic material is single-valued, and linear
 - No hysteresis loss
- Magnetic core has a very high μ_r , i.e. Core reluctance is negligible.
- No copper, no core losses (Efficiency $\eta = 100\%$)
- Interwinding capacitances are negligible at power frequencies (50Hz, 60Hz)

Basic Relations

1. From Faraday's Law: $e_1 = N_1 d\phi/dt$, and

$$e_2 = N_2 d\phi/dt$$

So,

$$\frac{e_1}{e_2} = \frac{N_1}{N_2}$$


2. Since winding resistances & leakage fluxes are negligible:

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

3. $\mathcal{F}_1 = \mathcal{F}_2$

$$\frac{i_1}{i_2} = \frac{N_2}{N_1}$$


4. Ideal transformer symbol

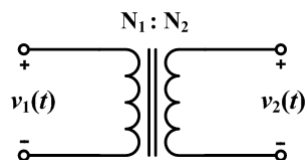


4. No power loss

Conservation of power: $v_1 i_1 = v_2 i_2$

5. Under Load

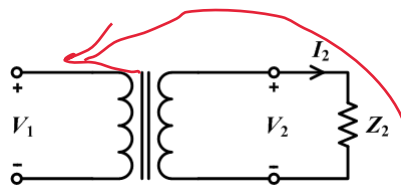

Ideal transformer under load

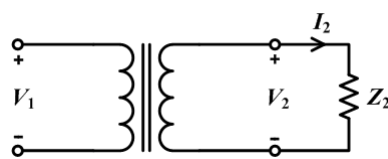


$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

$$\frac{i_1}{i_2} = \frac{N_2}{N_1}$$

$$v_1 i_1 = v_2 i_2$$

$$v_2 = i_2 Z_2$$

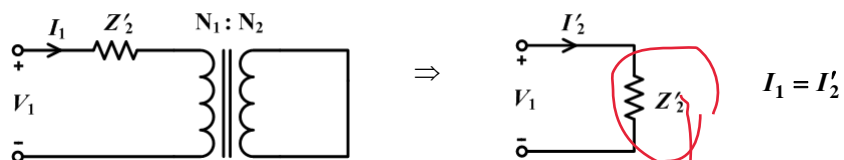

Eqv. crt. referred to primary

Secondary impedance referred to primary side:

$$Z'_2 = \left(\frac{N_1}{N_2} \right)^2 Z_2 = n^2 Z_2$$

Terminology

V_1, I_1, Z_1 : actual primary quantities

V_2, I_2, Z_2 : actual secondary quantities


V'_1, I'_1, Z'_1 : primary quantities referred to secondary side

V'_2, I'_2, Z'_2 : secondary quantities referred to primary side

$$V'_1 = \frac{N_2}{N_1} V_1, \quad I'_1 = \frac{N_1}{N_2} I_1, \quad Z'_1 = \left(\frac{N_2}{N_1} \right)^2 Z_1$$


$$V'_2 = \frac{N_1}{N_2} V_2, \quad I'_2 = \frac{N_2}{N_1} I_2, \quad Z'_2 = \left(\frac{N_1}{N_2} \right)^2 Z_2$$

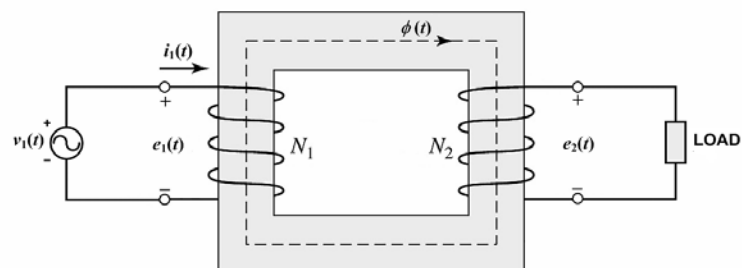3. Equivalent circuit representation of a practical transformer



Transformer under load

Equivalent Circuit representation

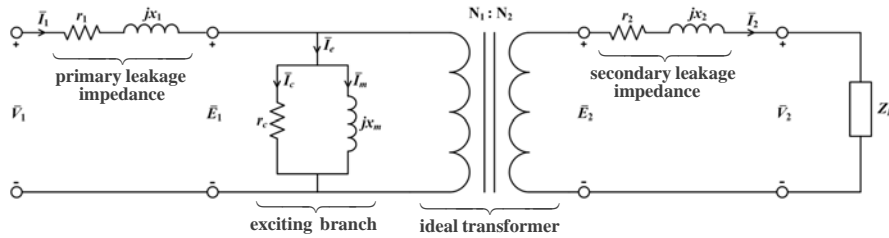


r_1 : Primary winding internal resistance (Ω) r_2 : Secondary winding internal resistance (Ω)

x_1 : Primary winding leakage reactance (Ω) x_2 : Secondary winding leakage reactance (Ω)

r_c : Core-loss resistance (Ω)

x_m : Magnetizing reactance (Ω)

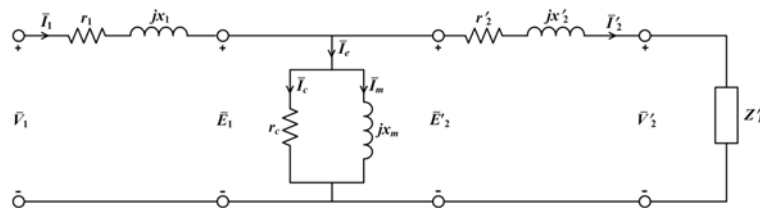Equivalent circuit referred to primary side



r'_2 : Secondary winding internal resistance referred to primary side

x'_2 : Secondary winding leakage reactance referred to primary side

I'_2 : Secondary winding current referred to primary side

V'_2 : Secondary winding voltage referred to primary side

Z'_L : Load impedance referred to primary side

$$r'_2 = n^2 r_2$$

$$x'_2 = n^2 x_2$$

$$I'_2 = \frac{I_2}{n}$$


$$V'_2 = n V_2$$

$$Z'_L = n^2 Z_L$$

$$n = \frac{N_1}{N_2}$$

$$E_1 = E'_2 = n E_2$$

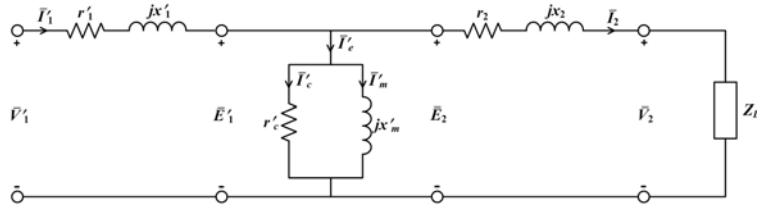Equivalent circuit referred to secondary side



r_1' : Primary winding internal resistance referred to secondary side

$$r_1' = \frac{r_1}{n^2}$$

$$n = \frac{N_1}{N_2}$$

x_1' : Primary winding leakage reactance referred to secondary side

$$x_1' = \frac{x_1}{n^2}$$

$$I_1' = nI_1$$

I_1' : Primary winding current referred to secondary side

V_1' : Primary winding voltage referred to secondary side

$$r_c' = \frac{r_c}{n^2}$$

$$V_1' = \frac{V_1}{n}$$


r_c' : Core-loss resistance referred to sec. side

$$x_m' = \frac{x_m}{n^2}$$

$$E_2 = E_1' = \frac{E_1}{n}$$

x_m' : Magnetizing reactance referred to sec. side

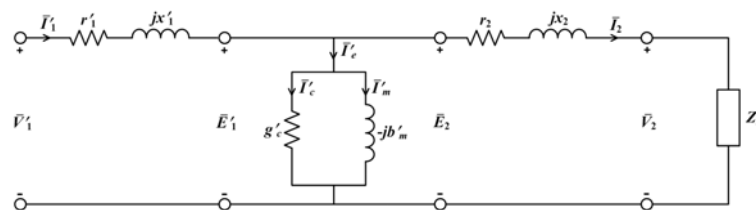Equivalent circuit referred to secondary side



g_c' : Core-loss conductance referred to sec. side

b_m' : Magnetizing admittance referred to sec. side

$$n = \frac{N_1}{N_2}$$


$$g_c' = \frac{1}{r_c'}$$

$$-jb_m' = \frac{1}{jx_m'}$$


$$g_c' = n^2 g_c$$

$$b_m' = n^2 b_m$$

Simplification

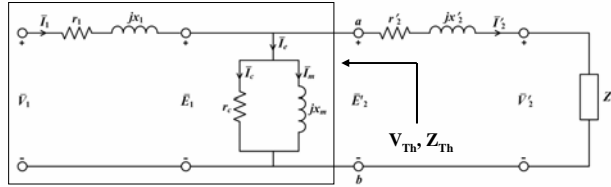

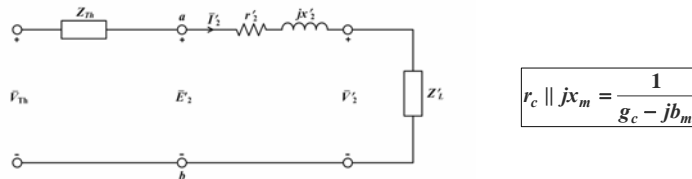Let us apply Thévenin equivalent circuit to the primary side



$$r_c \parallel jx_m = \frac{1}{g_c - jb_m}$$



$$\bar{V}_{Th} = \bar{V}_1 \frac{r_c \parallel jx_m}{(r_1 + jx_1) + (r_c \parallel jx_m)} \cong \bar{V}_1 \quad \text{where } |r_c \parallel jx_m| \gg |r_1 + jx_1|$$

$$\boxed{\bar{V}_{Th} \cong \bar{V}_1}$$

$$Z_{Th} = (r_1 + jx_1) \parallel (r_c \parallel jx_m) \cong r_1 + jx_1$$

$$\boxed{Z_{Th} \cong r_1 + jx_1}$$

Simplification

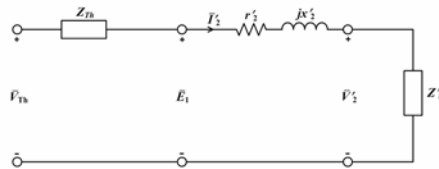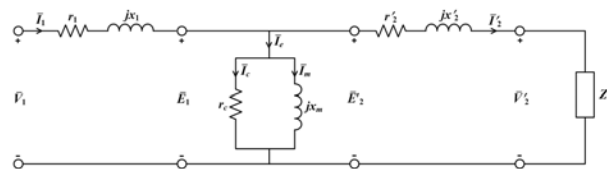


$$\bar{E}_1 = \bar{V}_{Th} - Z_{Th} \bar{I}_2 \cong \bar{V}_{Th} \cong \bar{V}_1 \quad \text{where } Z_{Th} \cong r_1 + jx_1$$


$$\boxed{\bar{E}_1 \cong \bar{V}_1}$$

Error made in approximations is at most 1% – 2% compared to actual values.

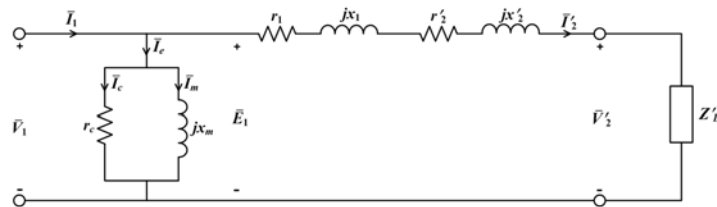
Approximate Equivalent Circuit referred to primary side



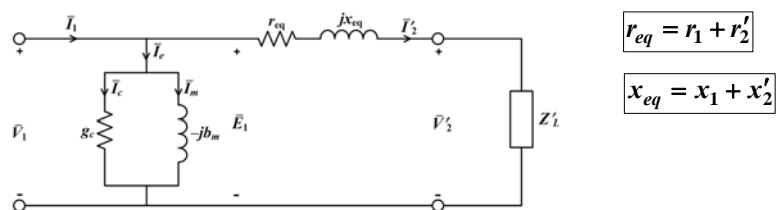
Further simplification gives us the figure below



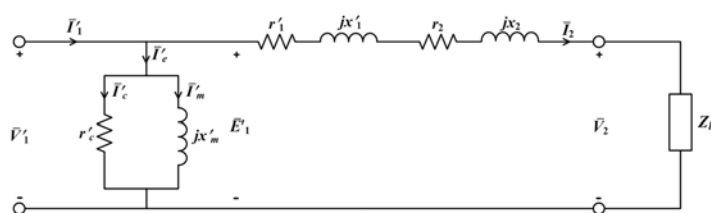Approximate Equivalent Circuit referred to secondary side




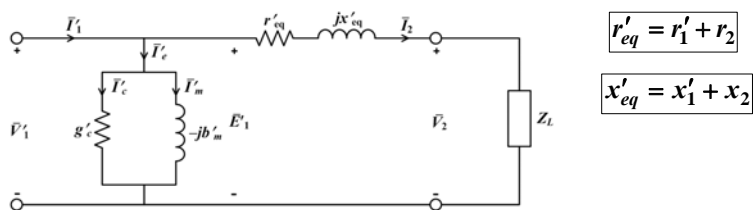Further simplification gives us the figure below




Approximate Equivalent Circuits for Large Transformers (referred to primary side)

(of a few 100 kVAs)

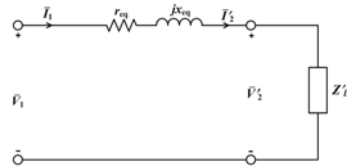


$|r_c \parallel jx_m|$ is very large

(in the MVA range)

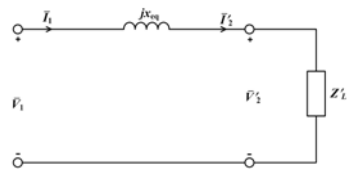

$x_{eq} \gg r_{eq}$ (4 - 10 times)

AC Power

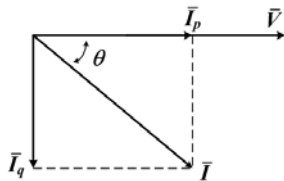

θ : angle between voltage \bar{V} and current \bar{I}

Real Power : $P = V_{\text{rms}} I_{\text{rms}} \cos \theta$ [W, Watts]


Reactive Power : $Q = V_{\text{rms}} I_{\text{rms}} \sin \theta$ [VAR, Volt Ampere Reactive]
(Imaginary Power)

Complex Power : $S = P + jQ$

Apparent Power : $|S| = V_{\text{rms}} I_{\text{rms}}$ [VA, Volt Ampere]

Power Factor : $\cos \theta = \frac{P}{|S|}$

Transformer Power Flow

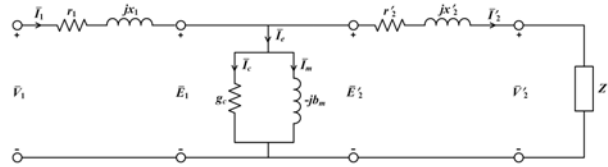

$$P_{\text{in}} = V_1 I_1 \cos \theta_1$$

$$P_{\text{out}} = P_{\text{load}} = V_2' I_2' \cos \theta_2$$

$$P_{\text{in}} = P_{\text{cu}_1} + P_{\text{core}} + P_{\text{cu}_2} + P_{\text{load}}$$

P_{cu} : Copper loss

P_{core} : Core loss

$$P_{\text{cu}_1} = I_1^2 r_1 = I_1'^2 r_1'$$

$$P_{\text{core}} = E_1^2 g_c = E_1'^2 g_c'$$


$$P_{\text{core}} \cong V_1^2 g_c$$

$$P_{\text{cu}_2} = I_2^2 r_2 = I_2'^2 r_2'$$


4. Short-circuit and Open-circuit Tests

- Measure voltage (V), current (I) and power (P) in order to determine the equivalent circuit parameters of the transformer:
 - For leakage impedance parameters
 - with secondary short circuited
 - For exciting branch parameters
 - with secondary open circuited


i. Short-circuit Test

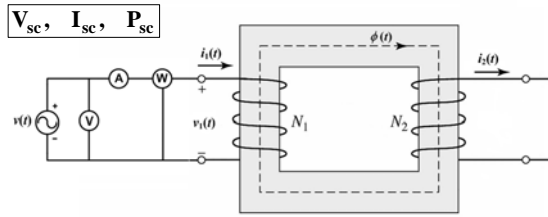

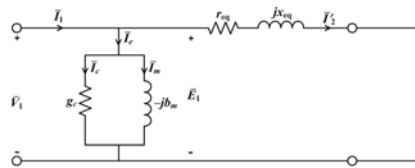A reduced voltage V_{sc} of 2% - 10% of rated voltage is applied to allow rated primary current.




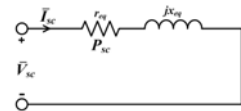where $\frac{1}{g_c - jb_m} \gg r_{eq} + jx_{eq}$



Short circuit equivalent circuit

Short-circuit Test

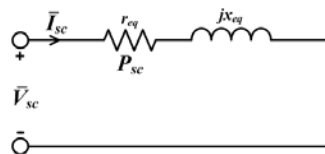

$$r_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$|z_{eq}| = \frac{V_{sc}}{I_{sc}}$$

where $z_{eq} = r_{eq} + jx_{eq}$

$$x_{eq} = \sqrt{|z_{eq}|^2 - r_{eq}^2}$$

$$r_{eq} = r_1 + r_2' \quad \text{where } r_1 \cong r_2'$$


$$r_1 = r_2' \cong \frac{r_{eq}}{2}$$

$$x_{eq} = x_1 + x_2' \quad \text{where } x_1 \cong x_2'$$


$$x_1 = x_2' \cong \frac{x_{eq}}{2}$$

at 50 Hz $r_{1AC} = 1.1 r_{1DC}$ ← Measured DC resistance
 $r_{2AC} = 1.1 r_{2DC}$ ← Measured DC resistance
 Form factor


ii. Open-circuit Test

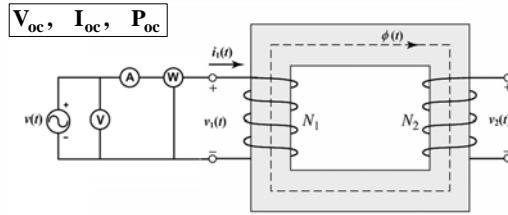

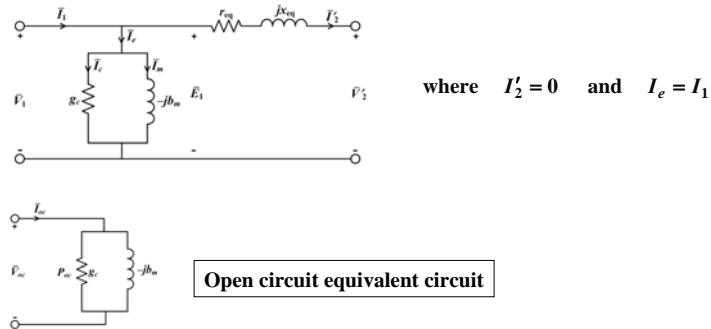Rated voltage is applied to the transformer under no-load and exciting current flows, which is a few percent of rated current.



Open-circuit Test

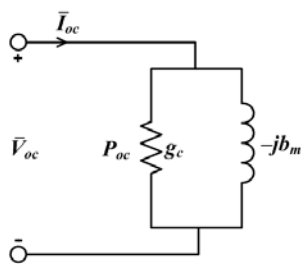

$$g_c = \frac{P_{oc}}{V_{oc}^2}$$

$$|Y_c| = \frac{I_{oc}}{V_{oc}}$$

where $Y_c = g_c - j b_m$

$$b_m = \sqrt{|Y_c|^2 - g_c^2}$$

where $g_c = \frac{1}{r_c}$ and $b_m = \frac{1}{x_m}$

5. Voltage regulation (VR%)


- The change in secondary terminal voltage (load voltage) from no-load to full-load
 - expressed as a percentage (%) of the rated value
 - ideally VR% = 0.

$$\text{VR}\% = \frac{V_1 - V_2'}{V_{1(\text{rated})}} \times 100\%$$

OR

$$\text{VR}\% = \frac{V_1' - V_2}{V_{2(\text{rated})}} \times 100\%$$


Simplification by approximation

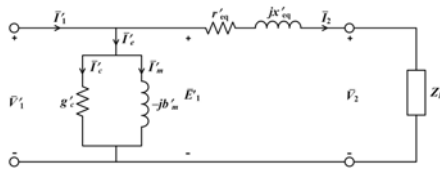

$$\bar{V}_1' = \bar{V}_2 + (r'_{eq} + j x'_{eq}) \bar{I}_2$$

$$V_1' \approx V_2 + I_2 r'_{eq} \cos \theta + I_2 x'_{eq} \sin \theta$$
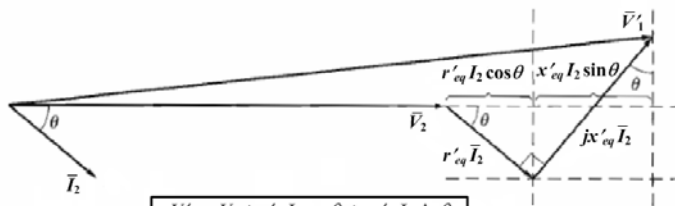
$$\text{VR}\% = \frac{I_2 r'_{eq} \cos \theta + I_2 x'_{eq} \sin \theta}{V_2} \times 100\%$$



$$V_1' \cong V_2 + r'_{eq} I_2 \cos \theta + x'_{eq} I_2 \sin \theta$$

Zero regulation, i.e. VR% = 0

- For zero regulation, phase angle (θ) of the load is given by

$$\text{VR}\% = \frac{I_2}{V_2} (r'_{eq} \cos \theta + x'_{eq} \sin \theta) \times 100\% \qquad r'_{eq} \cos \theta + x'_{eq} \sin \theta = 0$$

$$\theta = -\tan^{-1} \left(\frac{r'_{eq}}{x'_{eq}} \right)$$

Note that $\theta < 0$, so

Load must be capacitive for zero regulation

NOTE

- For an inductive load, $Z_L = R_L + jX_L$
 - Always $V'_1 > V_2$, i.e. $\text{VR}\% > 0$
- For a capacitive load, $Z_L = R_L - jX_L$
 - Usually $V'_1 \leq V_2$, i.e. $\text{VR}\% \leq 0$ (where $-x'_{eq} \sin \theta \geq r'_{eq} \cos \theta$)

6. Efficiency ($\eta\%$)

- The ratio of the output power given to the load and the input power taken from the electrical supply
 - expressed as a percentage (%)

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} 100\%$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{losses}}} 100\%$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{losses}}} 100\%$$

$$P_{\text{losses}} = P_{\text{cu}} + P_{\text{core}}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{cu}_1} + P_{\text{cu}_2} + P_{\text{core}}} 100\%$$

$$P_{\text{cu}} = P_{\text{cu}_1} + P_{\text{cu}_2}$$

$$\eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + I_1^2 r_1 + I_2^2 r_2 + V_1^2 g_c} 100\%$$

$$P_{\text{cu}} \approx I_2^2 r'_{eq}$$

$$\eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + I_2^2 r'_{eq} + V_1^2 g_c} 100\%$$

or

$$\eta = \frac{V_2' I_2' \cos \theta}{V_2' I_2' \cos \theta + I_2'^2 r_{eq} + V_1^2 g_c} 100\%$$

Maximum efficiency

Let us find the value of I_2 which maximizes the efficiency $\frac{d\eta}{dI_2} = 0$

$$\text{where } \eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + I_2^2 r'_{eq} + P_{core}} \cdot 100\%$$

$$\frac{d\eta}{dI_2} = 0 \Rightarrow V_2 \cos \theta (V_2 I_2 \cos \theta + I_2^2 r'_{eq} + P_{core}) - (V_2 \cos \theta + 2I_2 r'_{eq}) V_2 I_2 \cos \theta = 0$$

$$V_2 I_2 \cos \theta + I_2^2 r'_{eq} + P_{core} - (V_2 \cos \theta + 2I_2 r'_{eq}) I_2 = 0$$

$$P_{core} - I_2^2 r'_{eq} = 0$$

$$P_{core} = I_2^2 r'_{eq}$$

$$\boxed{P_{core} = P_{cu}}$$

$$\text{i.e., } V_1^2 g_c = I_2^2 r'_{eq} = I_2'^2 r_{eq}$$

Thus, maximum efficiency is achieved if core loss equals to the copper loss.

Examples

1. A 12kVA, 220/440V, 50 Hz single phase transformer has the following test data:
 - No-load test: 220V, 2A, 165W (measured at primary side)
 - Short-circuit test: 12V, 15A, 60W (measured at secondary side)
 - a) Calculate the equivalent circuit parameters referred to primary side
 - b) Calculate the primary terminal voltage on full-load at a power factor of: 0.8 pf lagging.

2. Given a 250kVA, 4160:480V, 60 Hz transformer, the following parameters are obtained by tests

- $r_1 = 0.09 \Omega$ and $x_1 = 1.7 \Omega$
- $r_2 = 1.2 \times 10^{-3} \Omega$ and $x_2 = 2.26 \times 10^{-2} \Omega$

Neglecting core losses,

- Calculate the primary voltage and voltage regulation for rated load at 76% pf lagging
- Repeat a) for a load of 76% pf leading
- Calculate the transformer efficiency for parts a) and b) with a core loss $P_{\text{core}} = 547\text{W}$.

3. The parameters of the exact equivalent circuit of a 150kVA, 2400/240V transformer are

- $r_1 = r'_2 = 0.2 \Omega$
- $x_1 = x'_2 = 0.45 \Omega$
- $r_c = 10 \text{ k}\Omega$ and $x_m = 1.55 \text{ k}\Omega$

Using both the exact and approximate equivalent circuit of the transformer, determine

- Voltage regulation
 - Efficiency
- for rated load at 0.8pf lagging

4. At 10kVA, 8000:230V transformer has a leakage impedance referred to primary of $90 + j400\Omega$. Exciting branch parameters are
- $r_c = 500\text{ k}\Omega$ and $x_m = 60\text{ k}\Omega$
- a) If primary voltage $V_1 = 7967\text{V}$ and actual load impedance $Z_L = 4.2 + j3.15\Omega$, find the secondary voltage of the transformer
- b) If the load is disconnected, and a capacitor of $-j6\Omega$ is connected in its place, what will be the load voltage?